

Introduction to Computers and Programming

Prof. I. K. Lundqvist


Lecture 16
April 28 2004

Today

- Boolean Logic
- Simplifying Formulae
- Constructing Logical Statements


Pictorial Representation of AND and OR

AND

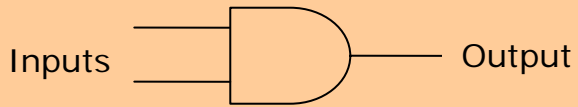

Inputs	Output
0 0	0
0 1	0
1 0	0
1 1	1


OR

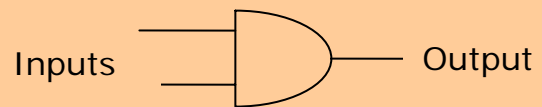

Inputs	Output
0 0	0
0 1	1
1 0	1
1 1	1


Pictorial Representation of XOR and NOT

XOR

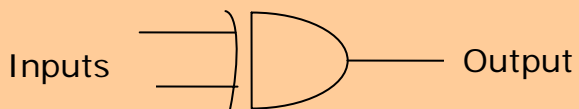

Inputs	Output
0 0	0
0 1	1
1 0	1
1 1	0

NOT

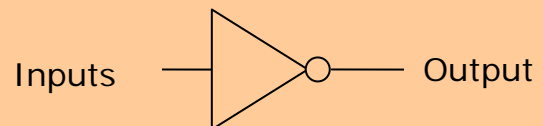

Inputs	Output
0	1
1	0


NAND and NOR

NAND



A	B	Out
0	0	1
0	1	1
1	0	1
1	1	0

NOR

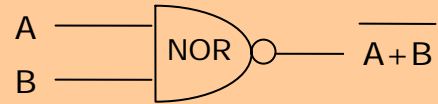

A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0

6

Proving DeMorgan's Theorem

$$\overline{(\overline{A} + \overline{B})} = \overline{\overline{A} \cdot \overline{B}}$$

A	B	\overline{A}	\overline{B}	$\overline{A} + \overline{B}$	$\overline{\overline{A} \cdot \overline{B}}$
0	0	1	1	1	0
0	1	1	0	1	0
1	0	0	1	1	0
1	1	0	0	0	1

$$\overline{(\overline{A} \cdot \overline{B})} = \overline{\overline{A} + \overline{B}}$$

PSET 😊 / ☹️

9

Truth Tables

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

Condition that A is 0, B is 0, C is 1.

$\bar{A} \cdot \bar{B} \cdot C$

$\bar{A} \cdot B \cdot \bar{C}$

$\bar{A} \cdot B \cdot C$

$A \cdot \bar{B} \cdot C$

$A \cdot B \cdot \bar{C}$

Function F is true if **any** of these and-terms are true!

OR

$$F = (\bar{A} \cdot \bar{B} \cdot C) + (\bar{A} \cdot B \cdot \bar{C}) + (\bar{A} \cdot B \cdot C) + (A \cdot \bar{B} \cdot C) + (A \cdot B \cdot \bar{C})$$

Sum-of-Products form

10

Minterms

- A **minterm** is a special product of literals, in which each input variable appears exactly once
- A function with **n** variables has **2^n minterms** (since each variable can appear complemented or not)
- A two-variable function, such as **$f(x,y)$** , has **$2^2 = 4$ minterms**

11

Example-1

A	B	C	Output
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

→ 4 minterms



$$\text{Output} = \bar{A} \cdot \bar{B} \cdot C + A \cdot \bar{B} \cdot C + A \cdot B \cdot \bar{C} + A \cdot B \cdot C$$

12

Boolean Algebra Theorems

$$A(BC) = (AB)C = A(BC), \quad A+B+C = (A+B)+C = A+(B+C)$$

AND, OR are associative

$$AB = BA, \quad A+B = B+A$$

AND, OR operations are commutative

$$A+BC = (A+B)(A+C), \quad A(B+C) = AB+AC$$

Forms of the distributive property

$$\overline{A+B} = \bar{A}\bar{B}$$

a form of DeMorgan's Theorem

$$\overline{AB} = \bar{A} + \bar{B}$$

a form of DeMorgan's Theorem

$$AA = A, \quad A+A = A, \quad \bar{A} + A = 1, \quad A\bar{A} = 0, \quad A = \bar{\bar{A}}$$

Single Variable Theorems

$$A + AB = A, \quad A + \bar{A}B = A + B$$

Two-variable theorems

$$A1 = A, \quad A+1 = 1, \quad A+0 = A, \quad A0 = 0, \quad \bar{1} = 0, \quad \bar{0} = 1$$

Identity and Null operations

13

Expression Simplification

Sum-of-Products Minimization

(Example-1)

$$A \cdot B \cdot \bar{C} + A \cdot B \cdot C + A \cdot \bar{B} \cdot C + \bar{A} \cdot \bar{B} \cdot C$$

$$\Rightarrow A \cdot B \cdot (\bar{C} + C) + \bar{B} \cdot C \cdot (A + \bar{A}) \quad [\text{distributive property}]$$

$$\Rightarrow A \cdot B \cdot 1 + \bar{B} \cdot C \cdot (A + \bar{A}) \quad [\text{single variable theorem}]$$

$$\Rightarrow A \cdot B \cdot 1 + \bar{B} \cdot C \cdot 1 \quad [\text{single variable theorem}]$$

$$\Rightarrow A \cdot B + \bar{B} \cdot C \cdot 1 \quad [\text{identity operation}]$$

$$\Rightarrow A \cdot B + \bar{B} \cdot C \quad [\text{identity operation}]$$

14

Karnaugh Maps

(Example-1)

Note: only 1 bit changes between adjacent cells

	AB	00	01	11	10
C	0	0	0	1	0
	1	1	0	1	1

$$\text{RED} = A \cdot B \cdot (\bar{C} + C) = A \cdot B$$

$$\text{GREEN} = C \cdot \bar{B} \cdot (\bar{A} + A) = C \cdot \bar{B}$$

$$\text{BLUE} = C \cdot (A \cdot B + A \cdot \bar{B}) = C \cdot A (B + \bar{B}) = C \cdot A$$

15

Karnaugh Maps (Example-1)

Note: only 1 bit changes between adjacent cells

		00	01	11	10
AB					
C	0	0	0	1	0
	1	1	0	1	1

$$\text{RED} = A \cdot B \cdot (\bar{C} + C) = A \cdot B$$

$$\Rightarrow A \cdot B + \bar{B} \cdot C$$

$$\text{GREEN} = C \cdot \bar{B} \cdot (\bar{A} + A) = C \cdot \bar{B}$$

16

2 Variable K-Maps

	A	0	1
B	0		
	1		



	A	0	1
B	0	$\bar{A}\bar{B}$	$A\bar{B}$
	1	$\bar{A}B$	AB

17

CQ 1

$$\bar{A}\bar{B} + A\bar{B}$$

I

		A	
		0	1
B	0	1	0
	1	1	0

III

		A	
		0	1
B	0	1	1
	1	0	0

II

		A	
		0	1
B	0	?	?
	1	?	?

IV

		A	
		0	1
B	0	1	1
	1	1	1

18

2 Variable K-Map Example

$$\bar{A}\cdot\bar{B} + \bar{A}\cdot B$$



		A	
		0	1
B	0	1	0
	1	1	0



\bar{A}

$$\begin{aligned} \bar{A}\cdot\bar{B} + \bar{A}\cdot B &= \bar{A}(\bar{B} + B) \\ &= \bar{A}\cdot 1 \\ &= \bar{A} \end{aligned}$$

[Distributive]
 [$B + \bar{B} = 1$]
 [$A \cdot 1 = A$]

19

Three Variable K-Map

	AB	00	01	11	10
C	0	1	0	1	0
	1	1	0	0	1



$$\bar{A} \cdot \bar{B} \cdot \bar{C} + \bar{A} \cdot \bar{B} \cdot C + A \cdot B \cdot \bar{C} + A \cdot \bar{B} \cdot C$$

20

K-Map Rules of Simplification

	AB	00	01	11	10
CD	00	0	1	0	0
	01	0	0	0	0
	11	0	0	0	0
	10	0	1	0	0

$\bar{A} \cdot B \cdot \bar{D}$

	AB	00	01	11	10
CD	00	1	1	0	0
	01	1	1	0	0
	11	1	1	0	0
	10	1	1	0	0

\bar{A}

	AB	00	01	11	10
CD	00	1	0	0	1
	01	0	0	0	0
	11	0	0	0	0
	10	1	0	0	1

$\bar{A} \cdot \bar{B}$

1. Circle the **largest groups possible**
2. Group dimensions must be a **power of 2**

Four Variable K-Maps Example-2

Using a 4-variable K-Map, simplify the following Truth table

A	B	C	D	Output
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	0

AB	00	01	11	10
CD 00	0	1	0	0
01	0	0	0	1
11	0	0	0	0
10	0	0	1	0

Output = $\bar{A}\bar{B}\bar{C}\bar{D}$ + $A\bar{B}\bar{C}\bar{D}$ + $AB\bar{C}\bar{D}$

23

Four Variable K-Maps Example-2

Using a 4-variable K-Map, simplify the following Truth table

A	B	C	D	Output
0	0	0	0	1
0	0	0	1	1
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	0
0	1	1	1	0
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	1

AB	00	01	11	10
CD 00	1	1	0	1
01	1	1	0	0
11	0	0	1	0
10	0	0	1	1

Output = $\bar{A}\bar{C}$ + ABC + $A\bar{B}\bar{D}$

25

Product-of-Sums from a Truth Table

A	B	C	F	\bar{F}
0	0	0	0	1
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	1	0
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

Find an expression for \bar{F}

$$\bar{F} = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C}$$

$$F = \overline{\bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C}}$$

$$F = \overline{\bar{A}\bar{B}\bar{C}} \cdot \overline{\bar{A}\bar{B}C} \cdot \overline{\bar{A}B\bar{C}}$$

$$F = (A+B+C) \cdot (A+B+\bar{C}) \cdot (A+\bar{B}+C)$$