

MASSACHUSETTS INSTITUTE OF TECHNOLOGY
Department of Electrical Engineering and Computer Science

**6.374: Analysis and Design of Digital Integrated Circuits
Using HSPICE**

Fall 2002

Issued: 9/10/02

I. Basic Usage of HSPICE and Awaves

Step 1.

Create an HSPICE file

All HSPICE files should have an .sp extension.

Type in athena prompt:

```
% emacs inv.sp &
```

Simple HSPICE file1:

```
-----
```

```
*CMOS Inverter - DC Sweep
```

```
* Netlist
```

```
* Define Voltage Sources
```

```
vdd 1 0 2.5
```

```
vin in 0 pvdd
```

```
* Define Transistors
```

```
m1 out in 1 1 pch l=0.25u w=1.125u as=0.7p ad=0.7p ps=2.375u pd=2.375u
```

```
m2 out in 0 0 nch l=0.25u w=0.375u as=0.7p ad=0.7p ps=2.375u pd=2.375u
```

```
* Define Output Capacitance
```

```
Cout out 0 30f
```

```
* Define Parameters
```

```
.param pvdd=2.5V
```

```
* Models
```

```
.lib 'logic025.l' TT
```

```
* Analysis
```

```
* post option necessary for awaves
```

```
.options nomod post
```

```

* DC sweep from 0 to 2.5V at 0.01V increments
.dc vin 0 pvdd 0.01

.end
-----

Simple HSPICE file2:
-----
*CMOS Inverter - Transient Analysis

* Netlist

* Define Voltage Sources
vdd 1 0 2.5
vin in 0 pulse(0v 2.5v 1n 0.1n 0.1n 4n 8n)

* Define Transistors
m1 out in 1 1 pch l=0.25u w=1.125u as=0.7p ad=0.7p ps=2.375u pd=2.375u
m2 out in 0 0 nch l=0.25u w=0.375u as=0.7p ad=0.7p ps=2.375u pd=2.375u

* Define Output Capacitance
Cout out 0 30f

* Models
.lib 'logic025.1' TT

* Analysis

* post option necessary for awaves
.options nomod post

* Transient Analysis for 10ns
.tran 0.01n 10n

.end
-----

```

There are three main sections in the file:

- a. the *netlist*: Netlist is a designation for a computer readable representation of the circuit schematic.
- b. the *models*: A model in spice is a description of the parameters of the equations used by spice to analyze the circuit.
- c. the *analysis* to be performed: here we are requesting a DC sweep from 0 to 2.5 with 0.01V increments and a transient analysis for 10 ns with step 0.01n.
- d. the *end* of the file. This isn't really a main section, but hspice won't work without it, and many people forget about it. Always put a .end statement at the end of your file.

Step 2.

If you haven't done so, add spice (this command also adds awaves):

```
% add hspice
```

Run spice in the background, and direct the output to a file for later reference:

```
% hspice inv.sp > inv.out &
```

When the simulation is complete, you should have some *.sw* (DC “sweep” data) and/or *.tr* (transient analysis data) files:

```
% ls
```

```
inv.sp      inv.out      inv.sw0      inv.tr0
```

Step 3.

Now, we use awaves to display the data generated by hspice stored in the .sw and .tr files:

```
% awaves inv &
```

To view waveforms, select the node number (or node name) that you want to see with the mouse button and drag and drop them in the highlighted panel. Double-clicking on the node numbers also brings up the waveforms. Panels are highlighted when they have a red border. The graph window will display the waveforms which can be measured using a variety of features.

NOTE: awaves doesn't run on Linux.