
***Lumped-element Modeling
with Equivalent Circuits***

Joel Voldman

Massachusetts Institute of Technology

Outline

- > **Context and motivation**
- > **Lumped-element modeling**
- > **Equivalent circuits and circuit elements**
- > **Connection laws**

Context

> Where are we?

- We have just learned how to make structures
- About the properties of the constituent materials
- And about elements in two domains
 - » structures and electronics

> Now we are going to learn about modeling

- Modeling for arbitrary energy domains
- How to exchange energy between domains
 - » Especially electrical and mechanical
- How to model dynamics

> After, we start to learn about the rest of the domains

Inertial MEMS

> Analog Devices Accelerometer

- ADXL150
- Acceleration → Changes gap → capacitance → electrical output

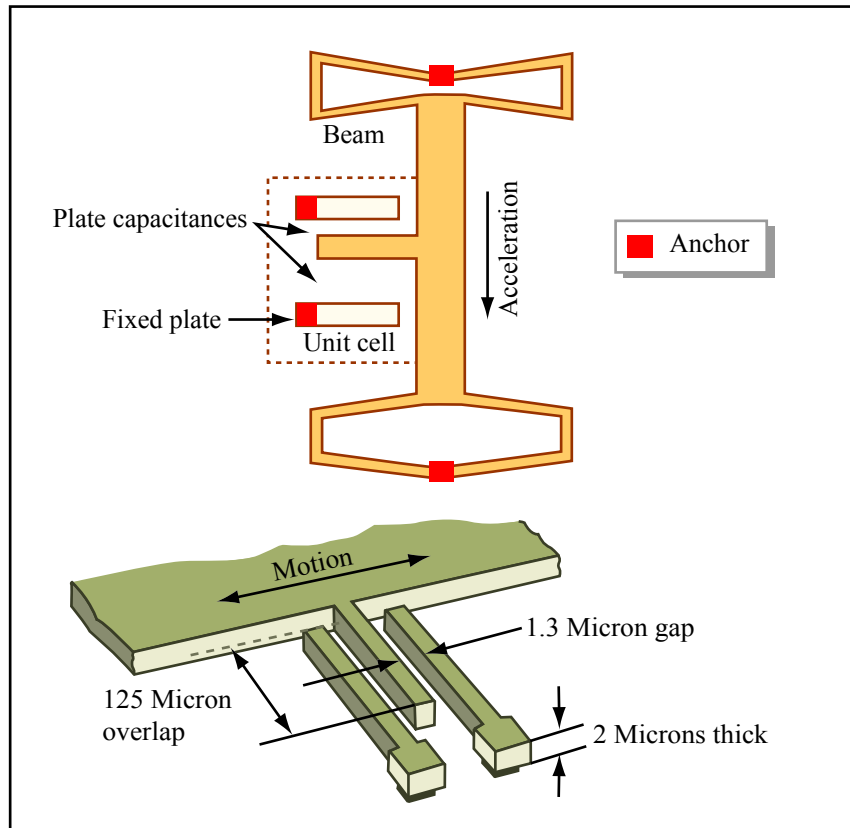


Image removed due to copyright restrictions.
Photograph of a circuit board.

Image removed due to copyright restrictions.
Micrograph of machined microchannels.

Image by MIT OpenCourseWare.

RF MEMS

- > Use electrical signal to create mechanical motion
- > Series RF Switch (Northeastern & ADI)
 - Cantilever closes circuit when actuated → relay

Image removed due to copyright restrictions.

Image removed due to copyright restrictions.

Figure 11 on p. 342 in: Zavracky, P. M., N. E. McGruer, R. H. Morrison, and D. Potter. "Microswitches and Microrelays with a View Toward Microwave Applications." *International Journal of RF and Microwave Computer-Aided Engineering* 9, no. 4 (1999): 338-347.

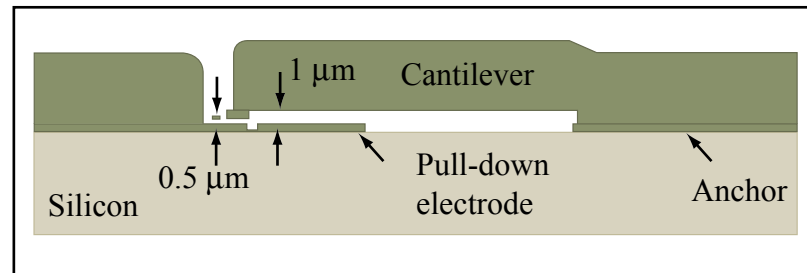


Image by MIT OpenCourseWare.

Adapted from Rebeiz, Gabriel *MRF MEMS: Theory, Design, and Technology*. Hoboken, NJ: John Wiley, 2003. ISBN: 9780471201694.

Zavracky et al., *Int. J. RF Microwave CAE*, 9:338, 1999, via Rebeiz *RF MEMS*

What we'd like to do

- > These systems are complicated 3D geometries
- > Transform electrical energy \leftrightarrow mechanical energy
- > How do we design such structures?
 - Multiphysics FEM
 - » Solve constitutive equations at each node
 - » Tedious but potentially most accurate
- > Is there an easier way?
 - That will capture dimensional dependencies?
 - Allow for quick iterative design?
 - Maybe get us within 10-20%?

Image removed due to copyright restrictions.

Distorted switch (Coventor)

RF MEMS Switch

> What we'd really like to know

- What voltage will close the switch?
- What voltage will open the switch (when closed)?
- How fast will this happen?
- What are the tradeoffs between these variables?
 - » Actuation voltage vs. maximum switching frequency

> So let's restrict ourselves to relations between voltage and tip deflection

- Hah! – we have “lumped” our system

Outline

- > Context and motivation
- > Lumped-element modeling
- > Equivalent circuits and circuit elements
- > Connection laws

Lumped-element modeling

> What is a lumped element?

- A discrete object that can exchange energy with other objects
- An object whose internal physics can be combined into terminal relations
- Whose size is smaller than wavelength of the appropriate signal
 - » Signals do not take time to propagate

Lumped elements

> Electrical capacitor


> Spring

> Rigid mass

- Push on it and it moves
- Relation between force and displacement


> Fluidic channel

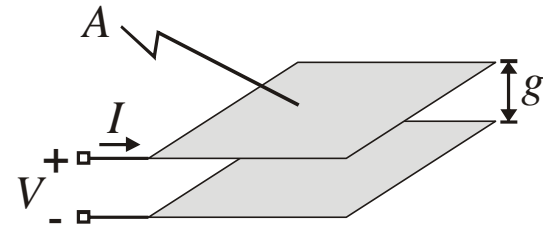- Apply pressure and fluid flows instantaneously
- Relation between pressure and volumetric flow rate



$$I = C \frac{dV}{dt}$$

Point Load

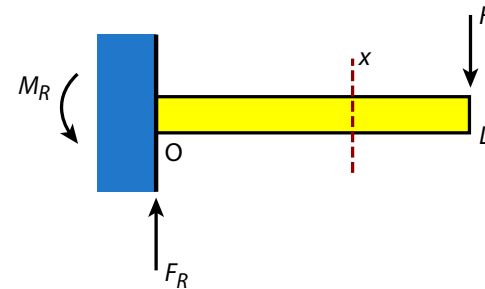

$$w_{\max} = \frac{1}{k_{\text{cantilever}}} F$$

Image by MIT OpenCourseWare.

Adapted from Figure 9.7 in: Senturia, Stephen D. *Microsystem Design*. Boston, MA: Kluwer Academic Publishers, 2001, p. 209. ISBN: 9780792372462.

Pros/cons of lumped elements

> Pros

- Simplified representations that carry dimensional dependencies
- Can do equivalent circuits
- Static and dynamic analyses

> Cons

- Lose information
 - » Deflection along length of cantilever
- Will not get things completely right
 - » Capacitance due to fringing fields

So how do we go about lumping?

> First, we need input/output relations

- This requires solving physics
- This is what we do in the individual domains
 - » We have already done this in electrical and mechanical domains


> For cantilever RF switch

- What is relation between force and tip deflection?
- Not voltage and deflection
 - » Different energy domains

RF Switch mechanical model

> We have seen that there is a linear relation between force and tip deflection

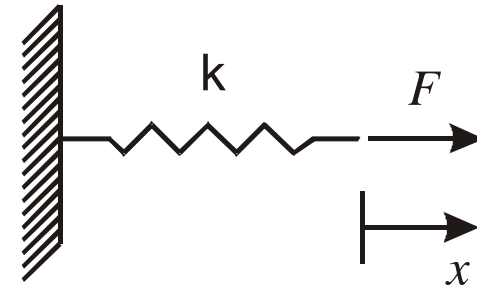- Cantilever behaves as linear spring k
- CAVEAT: k is specific for this problem
- Different k 's for same cantilever but
 - » Distributed force applied over whole cantilever
 - » Point force applied at end
 - » Deflection of cantilever middle is needed
 - » Etc.



$$F = kx$$

> Lesson: Don't just use equation out of a book


RF Switch mechanical model

> What else is needed for model?


> Inertia of cantilever →
Lumped mass

> Energy loss → Lumped dashpot

- Due to air damping

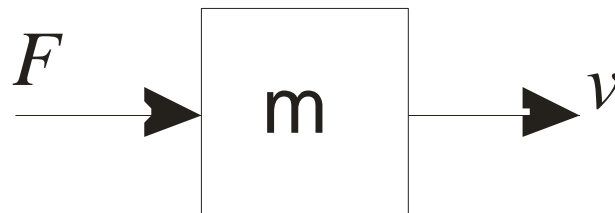
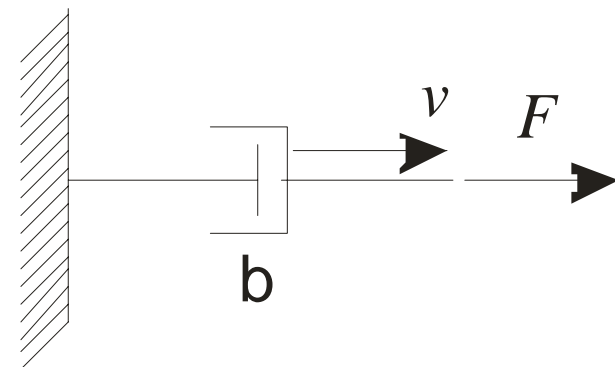
$$F = ma = m \frac{dv}{dt} = m \frac{d^2 x}{dt^2}$$




$$F = bv = b \frac{dx}{dt}$$

How do we connect these together?

> Intuition and physics
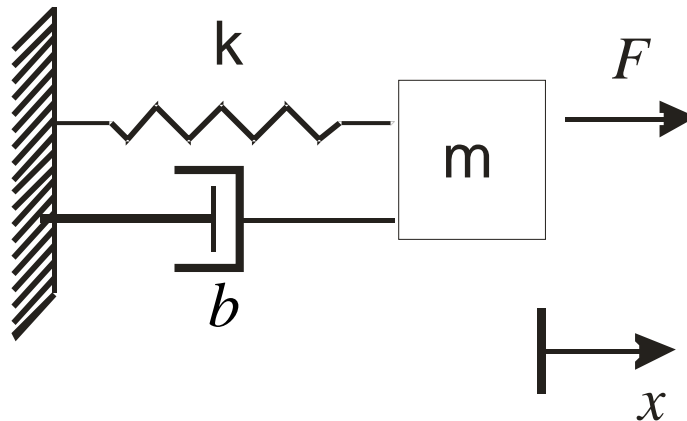
> Example: cantilever switch

- Tip movement (x) stretches spring
- And causes damping
- Tip has mass associated with it
- All elements have same displacement



Outline

- > Context and motivation
- > Lumped-element modeling
- > **Equivalent circuits and circuit elements**
- > Connection laws

Why use equivalent circuits?

> One modeling approach


- Use circuits for electrical domain
 - » Solve via KCL, KVL
- Use mechanical lumped elements in mechanical domain
 - » Solve via Newton's laws
- Connect two using ODEs or matrices or other representation

> Our approach

- Lumped elements have electrical equivalents
- Can hook them together such that solving circuit intrinsically solves Newton's laws (or continuity relationships)
- Now we have ONE representation for many different domains
- VERY POWERFUL

Onward to equivalent circuits

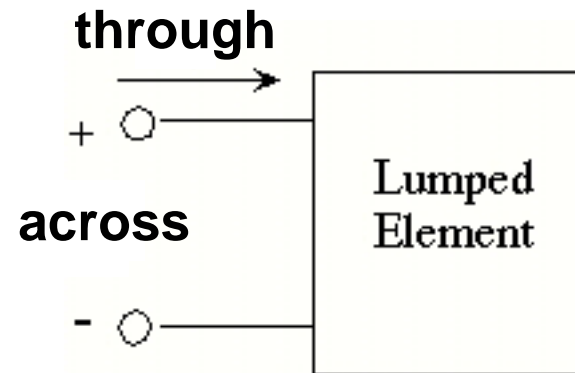- > Each lumped element has one or more ports
- > Each port is associated with two variables
 - A “through” variable
 - An “across” variable
- > Power into the port is defined by the product of these two variables



Onward to equivalent circuits

- > In electrical circuits, voltage is physically “across” and current is physically “through”

voltage → across

current → through

- > What happens when we *translate* mechanics into equivalent circuits?

force → across (V)

velocity → through (I)

OR

force → through (I)


velocity → across (V)

- > Why does this matter?

What circuit element is the spring?

- > It stores elastic energy
- > Is it a capacitor or an inductor?

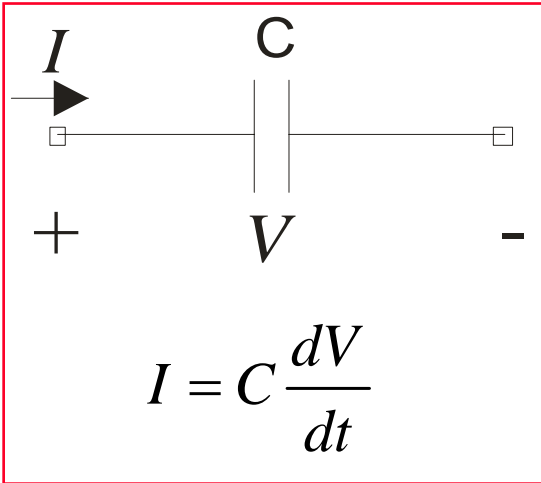force → across (V)
velocity → through (I)




$$F = k \int \dot{x} dt$$

$$L = \frac{1}{k}$$

$$F = kx$$

$$x = \frac{1}{k} F$$

$$\dot{x} = \frac{1}{k} \frac{dF}{dt}$$

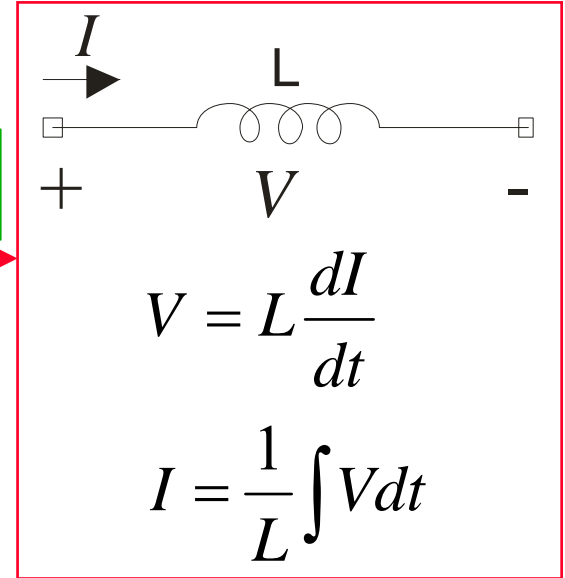

force → through (I)
velocity → across (V)

Which is correct?

- > Both are correct
- > And both are used → beware!
- > Velocity → voltage
 - “Indirect” or “mobility” analogy
 - Cleaner match between physical system and circuit
 - » Velocity is naturally “across” (e.g., relative) variable
 - But stores mechanical PE in inductors, KE in capacitors
 - Springs → Inductors
- > Force → voltage
 - “Direct” analogy
 - Always store PE in capacitors
 - Springs → Capacitors
- > Circuit topologies are dual of each other

**This is
what we
will use**

Generalized variables

- > We want a consistent modeling approach across different domains
- > Can we generalize what we just did?
 - » YES

Generalized variables

- > Formalize “terminal” relations
- > Displacement $q(t)$
- > Flow $f(t)$: the derivative of displacement
- > Effort $e(t)$
- > Momentum $p(t)$: the integral of effort
- > Net power into device is effort times flow

General

$$f = \frac{dq}{dt}$$

$$q = q_o + \int_0^t f dt$$

$$e = \frac{dp}{dt}$$

$$p = p_o + \int_0^t e dt$$

Mechanical

$$v = \frac{dx}{dt}$$

$$x = x_o + \int_0^t v dt$$

$$F = \frac{dp}{dt}$$

$$p = p_o + \int_0^t F dt$$

$$P_{net} = e \cdot f$$

Examples

> Effort-flow relations occur in MANY different energy domains

General	Electrical	Mechanical	Fluidic	Thermal
Effort (e)	Voltage, V	Force, F	Pressure, P	Temp. diff., ΔT
Flow (f)	Current, I	Velocity, v	Vol. flow rate, Q	Heat flow
Displacement (q)	Charge, Q	Displacement, x	Volume, V	Heat, Q
Momentum (p)	-	Momentum, p	Pressure Momentum, Γ	-
Resistance	Resistor, R	Damper, b	Fluidic resistance, R	Thermal resistance, R
Capacitance	Capacitor, C	Spring, k	Fluid capacitance, C	Heat capacity, mcp
Inertance	Inductor, L	Mass, m	Inertance, M	-
Node law	KCL	Continuity of space	Mass conservation	Heat energy conservation
Mesh law	KVL	Newton's 2 nd law	Pressure is relative	Temperature is relative

Other conventions

- > Thermal convention: T becomes the across variable (voltage) and heat-flow becomes the through variable (current)**
 - Conserved quantity is heat energy**

Building equivalent circuits

- > **Need power sources**
- > **Passive elements**
- > **Topology and connection rules**
 - **Figure out how to put things together**

- > **What do we get?**
 - **An intuitive representation of the relevant physics**
 - **Ability to model many domains in one representation**
 - **Access to *extremely* mature circuit analysis techniques and software**

One-port source elements



> Effort source and flow source

> Effort source establishes a time-dependent effort independent of flow

- Electrical voltage source
- Pressure source




> Flow source establishes a time-dependent flow independent of effort

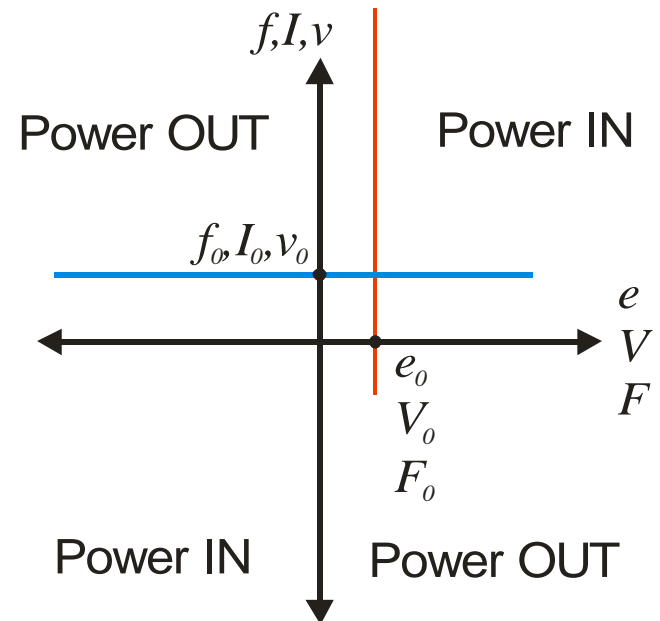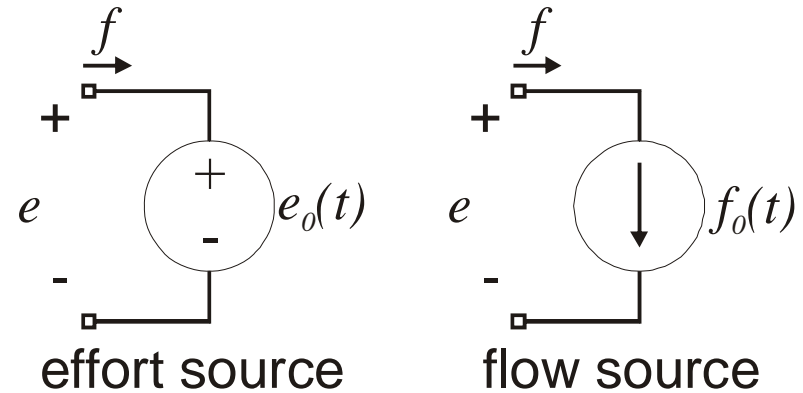- Electrical current source
- Syringe pump



One-port circuit elements

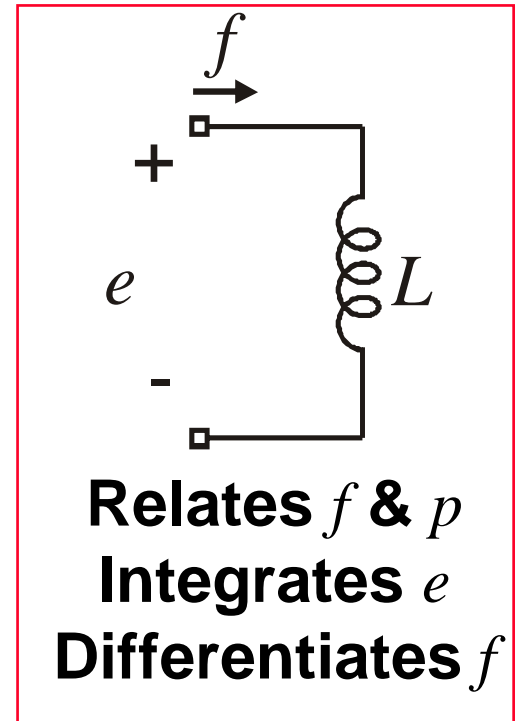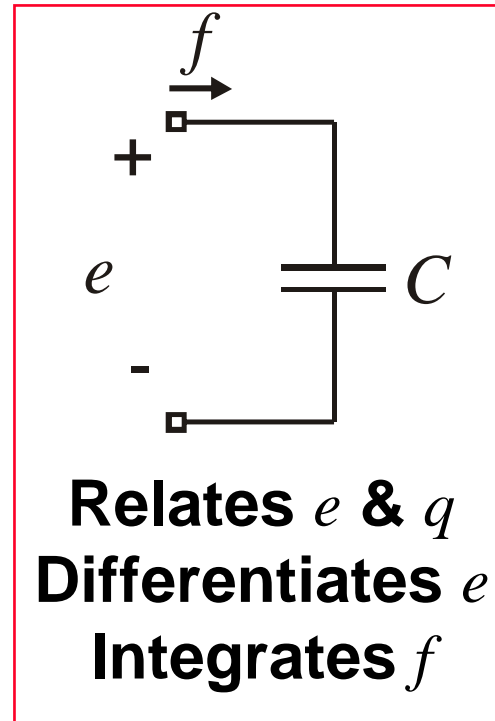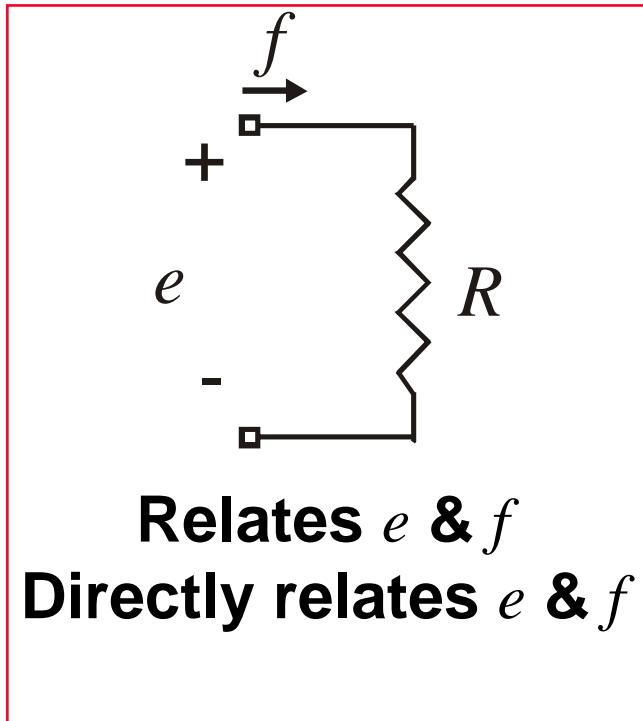
- > Three general passive elements
- > Represent different functional relationships
 - Energy storage, dissipation



Analogies between mechanics and electronics

> Electrical Domain

- A resistor

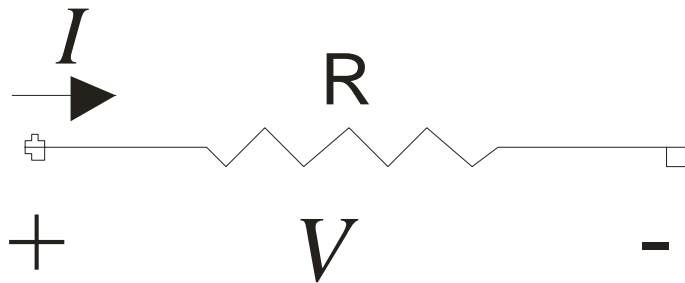


$$V = RI = R \frac{dQ}{dt}$$

$$R = b$$

> Mechanical Domain

- A damper (dashpot)

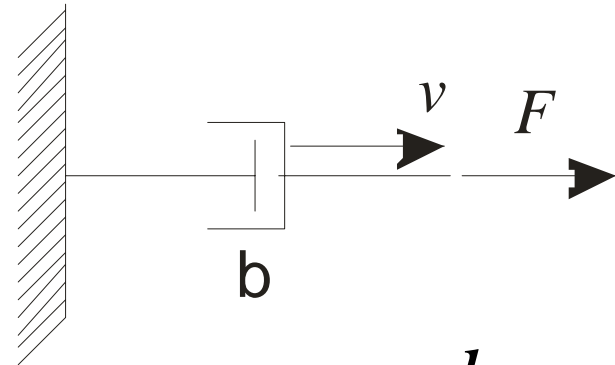

$$F = bv = b \frac{dx}{dt}$$

> There is again a correspondence between

- V and F
- I and v
- Q and x
- R and b


> $Electrical\ Power = VI$

> $Mechanical\ Power = Fv$

Generalized resistor

> For the resistor,

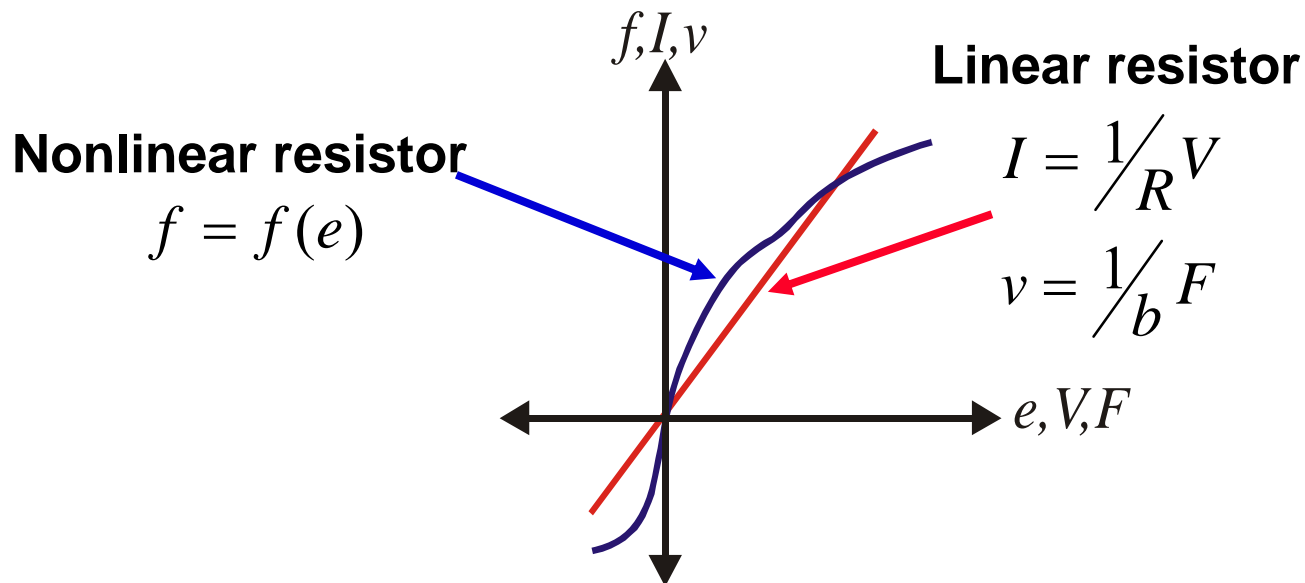
- e is an algebraic function of f (or vice versa)
- Can be a nonlinear function



Analogies between mechanics and electronics

> Electrical Domain

- A capacitor

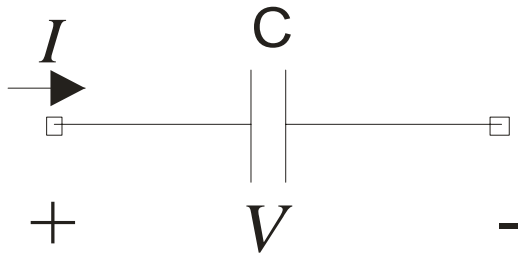


$$Q = CV$$

$$I = C \frac{dV}{dt}$$

$$C = \frac{1}{k}$$

> Mechanical Domain

- A spring

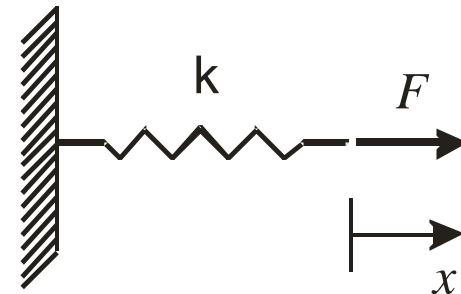

$$x = \frac{1}{k} F$$

$$\frac{dx}{dt} = \dot{x} = \frac{1}{k} \frac{dF}{dt}$$

> There is again a correspondence between


- V and F
- I and v
- Q and x
- R and b

> $Electrical\ Power = VI$

> $Mechanical\ Power = Fv$

Generalized capacitance

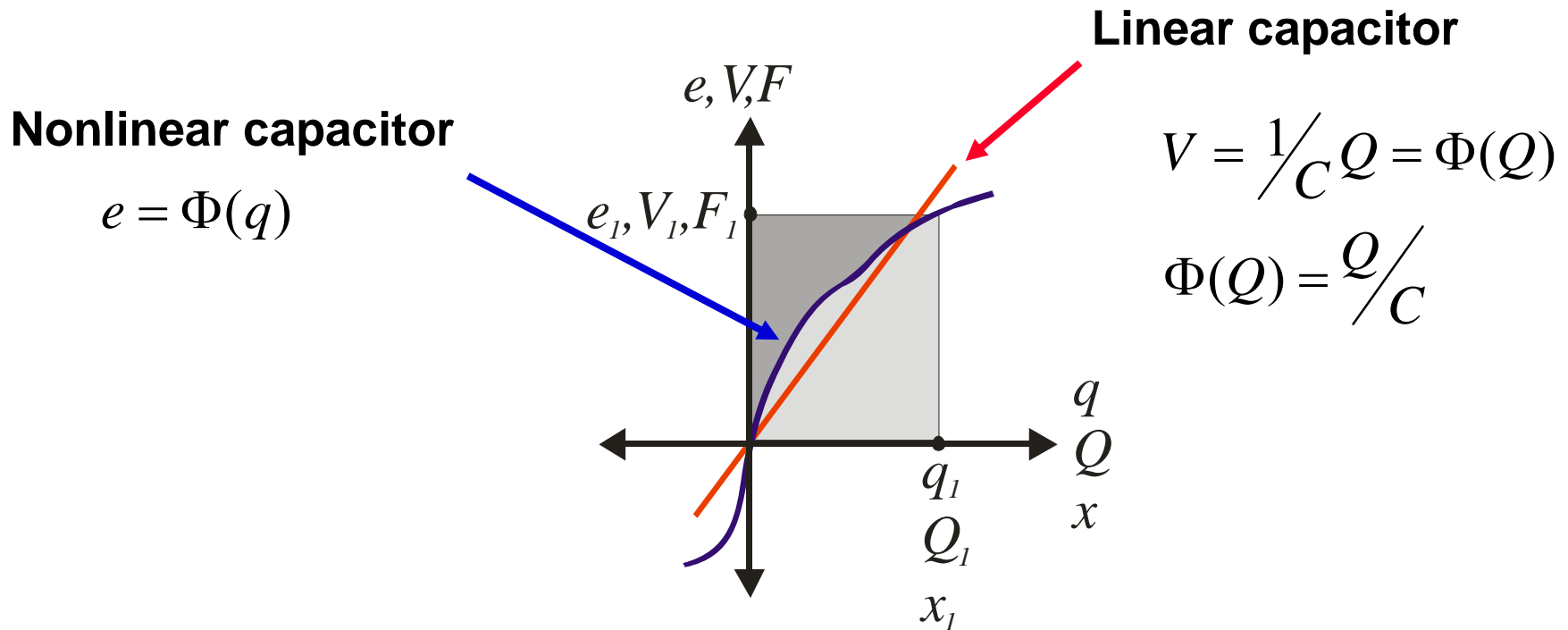- > For a generalized capacitance, the effort e is a function of the generalized displacement q .



Generalized capacitance

- > Capacitors store potential energy → How much?
- > Leads to concept of energy and co-energy

Energy

$$W(q_1) = \int_0^{q_1} e dq = \int_0^{q_1} \Phi(q) dq$$

Co-energy


$$W^*(e_1) = \int_0^{e_1} q de$$

$$= \int_0^{e_1} \Phi^{-1}(e) de$$

$$W(q_1) + W^*(e_1) = e_1 q_1$$

⇓

$$W^*(e_1) = e_1 q_1 - W(q_1)$$

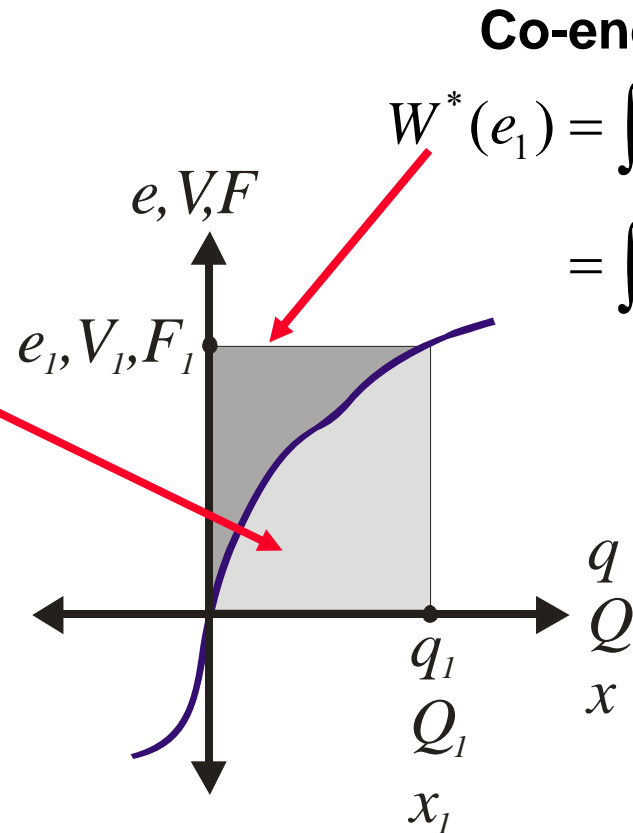

Parallel-plate capacitor


- > A linear parallel-plate capacitor
- > It's energy and co-energy are numerically equal

$$C = \frac{\epsilon A}{g}$$

$$V = \Phi(Q) = Q/C$$

$$W(Q) = \int_0^{Q_1} \Phi(Q) dQ = \int_0^{Q_1} Q/C dQ$$

$$W(Q) = \frac{Q^2}{2C}$$

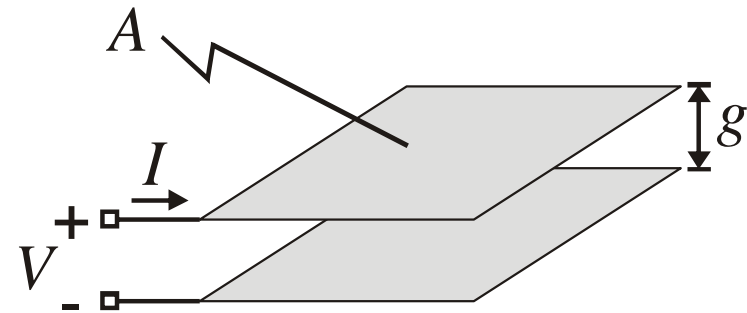

$$Q = \Phi^{-1}(V) = CV$$


$$W^*(V) = \int_0^{V_1} \Phi^{-1}(V) dV = \int_0^{V_1} CV dV$$

$$W^*(V) = \frac{CV^2}{2}$$

Analogies between mechanics and electronics


> Electrical Domain

- An inductor

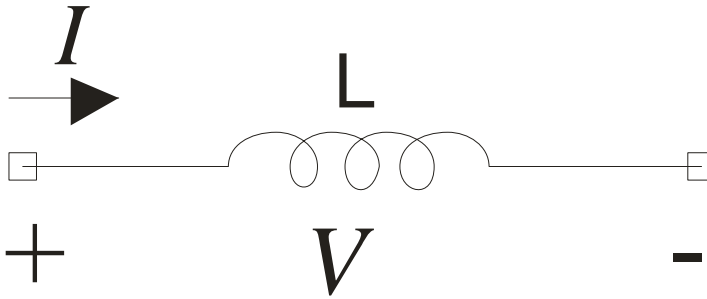

> Mechanical Domain

- A mass

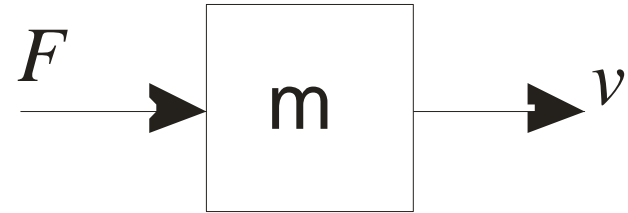

$$V = L \frac{dI}{dt} = L \frac{d^2 Q}{dt^2} \quad \boxed{L = m} \quad F = ma = m \frac{dv}{dt} = m \frac{d^2 x}{dt^2}$$

> There is a correspondence between

- V and F
- I and v
- Q and x
- L and m

> *Electrical Power* = VI

> *Mechanical Power* = Fv

Generalized Inertance

- > For a generalized inertance, flow f is a function of momentum p .
- > This once again leads to concepts of energy and co-energy


$$W(p_1) = \int_0^{p_1} f dp$$

$$W^*(f_1) = \int_0^{f_1} p df$$

$$W(p_1) + W^*(f_1) = f_1 p_1$$

⇓

$$W^*(f_1) = f_1 p_1 - W(p_1)$$

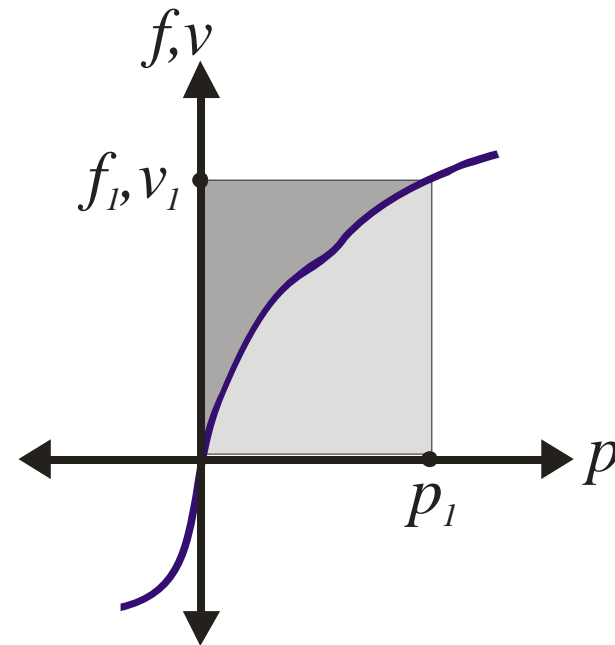


Outline


- > Context and motivation
- > Lumped-element modeling
- > Equivalent circuits and circuit elements
- > Connection laws

Circuits in the $e \rightarrow V$ convention

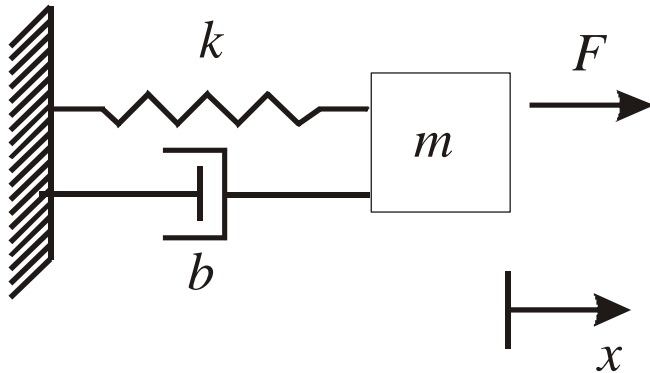- > Elements that share flow (e.g., current) and displacement (e.g., charge) are placed in series in an electric circuit
- > Elements that share a common effort (e.g., Voltage) are placed in parallel in an electric circuit




Spring-mass-dashpot system

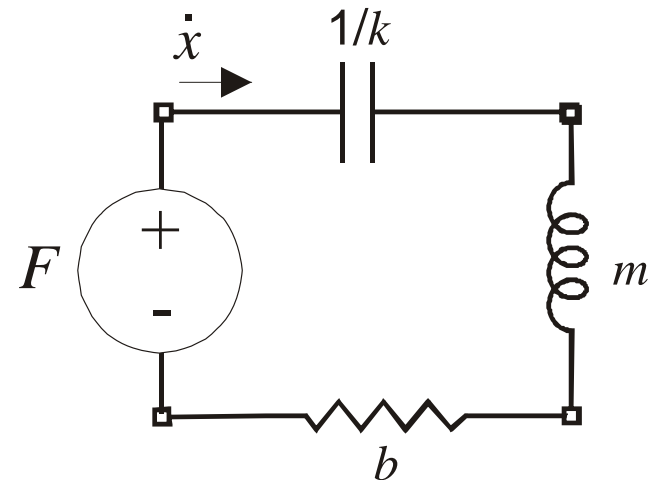

Equivalent circuit

Solving circuit solves the physics

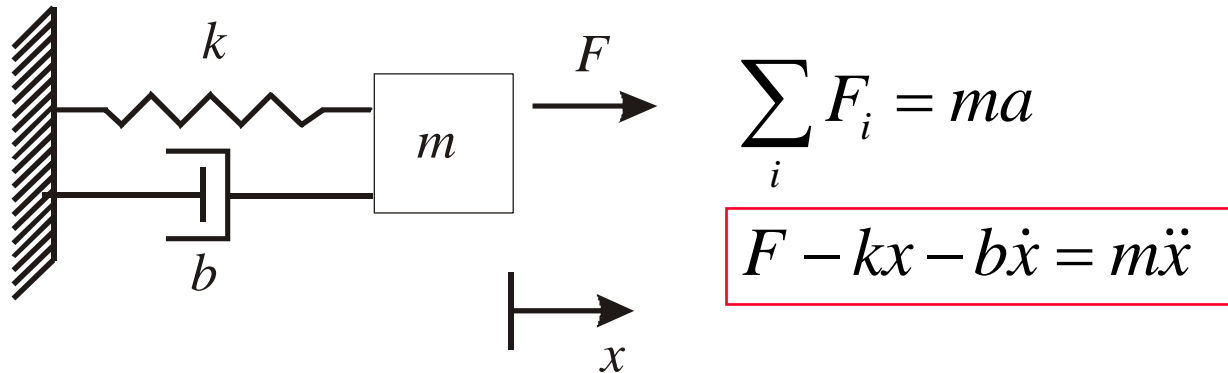- > Apply force balance to spring-mass-damper system




- > Solving KVL gives same result as Newton's laws!

$$F - F_k - F_m - F_b = 0$$

$$F_k = kx, F_b = b\dot{x}, F_m = m\ddot{x}$$

$$F = kx + b\dot{x} + m\ddot{x}$$

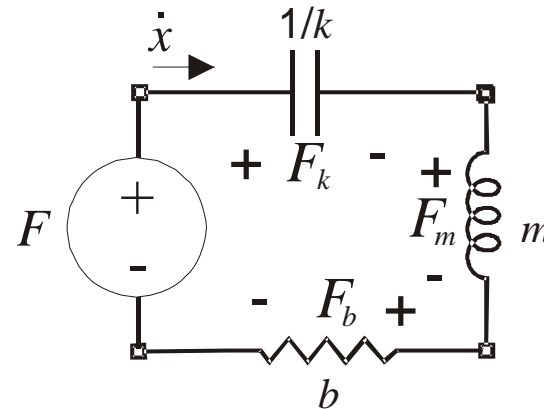

- > Can also do this with complex impedances

Generating equivalent circuits

> Possible to go “directly”




- But hard with $e \rightarrow V$ analogy
- See slide at end and text for details

> Easier to do via circuit duals

> Use convenience of $f \rightarrow V$ convention, then switch to $e \rightarrow V$

- Force is current source
- Each displacement variable is a node
- Masses connected between nodes and ground
- Other elements connected as shown in diagram

Example

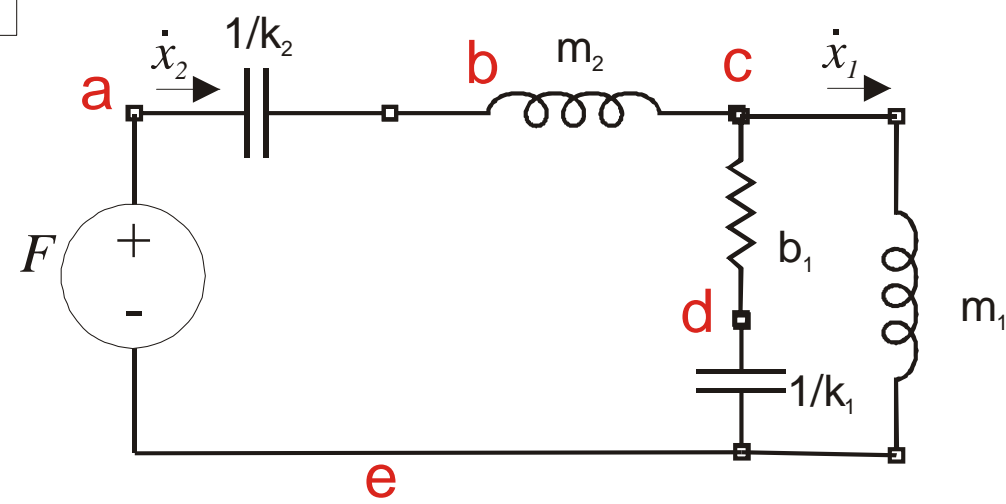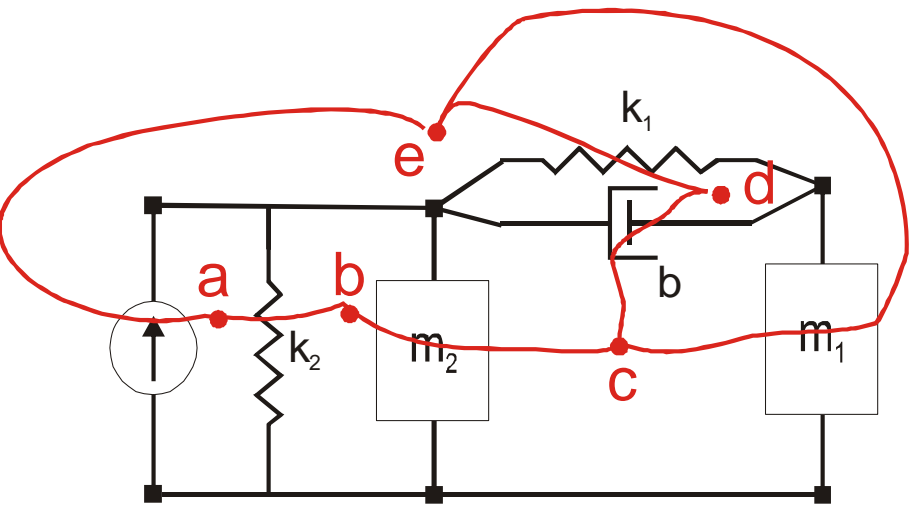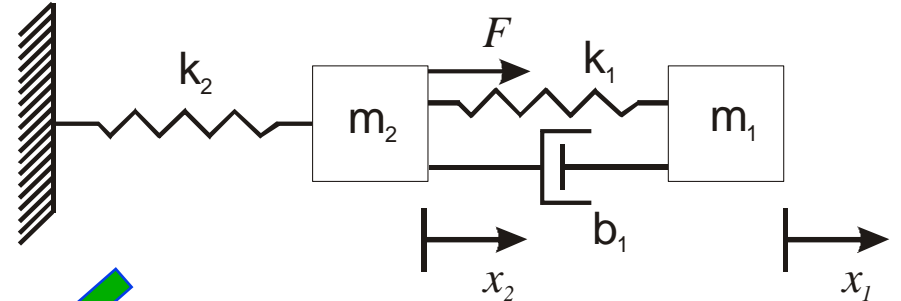

Where does this leave us?

- > A 2nd-order system is a 2nd-order system
- > Analogies between RLC and SMD system

$$\omega_n = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{m \frac{1}{k}}} = \sqrt{\frac{k}{m}}$$

- > Use what you already know to understand the intricacies of what you don't know

Energy coupling

- > Where is coupling between domains?
- > How does voltage \rightarrow deflection?
- > We need transducers \rightarrow two-port elements that store energy
- > We will do this next time...

Conclusion

- > **Can model complicated systems with lumped elements**
- > **Lumped elements from different domains have equivalent-circuit representations**
- > **These representations are not unique**
 - **We use the $e \rightarrow V$ convention in assigning voltage to the effort variable**
- > **Once we have circuits, we have access to POWERFUL analysis tools**

For more info

- > **Course text chapter 5**
- > **H.A.C. Tilmans. “Equivalent circuit representation of electromechanical transducers”**
 - **Part I: lumped elements: *J. Micromech. Microeng.* 6:157, 1996.**
 - **Part II: distributed systems: *J. Micromech. Microeng.* 7:285, 1997.**
 - **Errata: *J. Micromech. Microeng.* 6:359, 1996.**
- > **R. A. Johnson. *Mechanical filters in electronics***
- > **Woodson and Melcher. *Electromechanical Dynamics***
- > **M. Rossi. *Acoustics and electroacoustics***
- > **Lots and lots of papers**

Finding equivalent circuit: direct approach

> Find $e \rightarrow V$ equivalent circuit of following

> Note:

- k_2 and m_2 share same displacement, caused by F
- b_1 , and k_1 share same displacement, $x_2 - x_1$
- If $k_1 \rightarrow \infty$, m_2 and m_1 share same displacement

